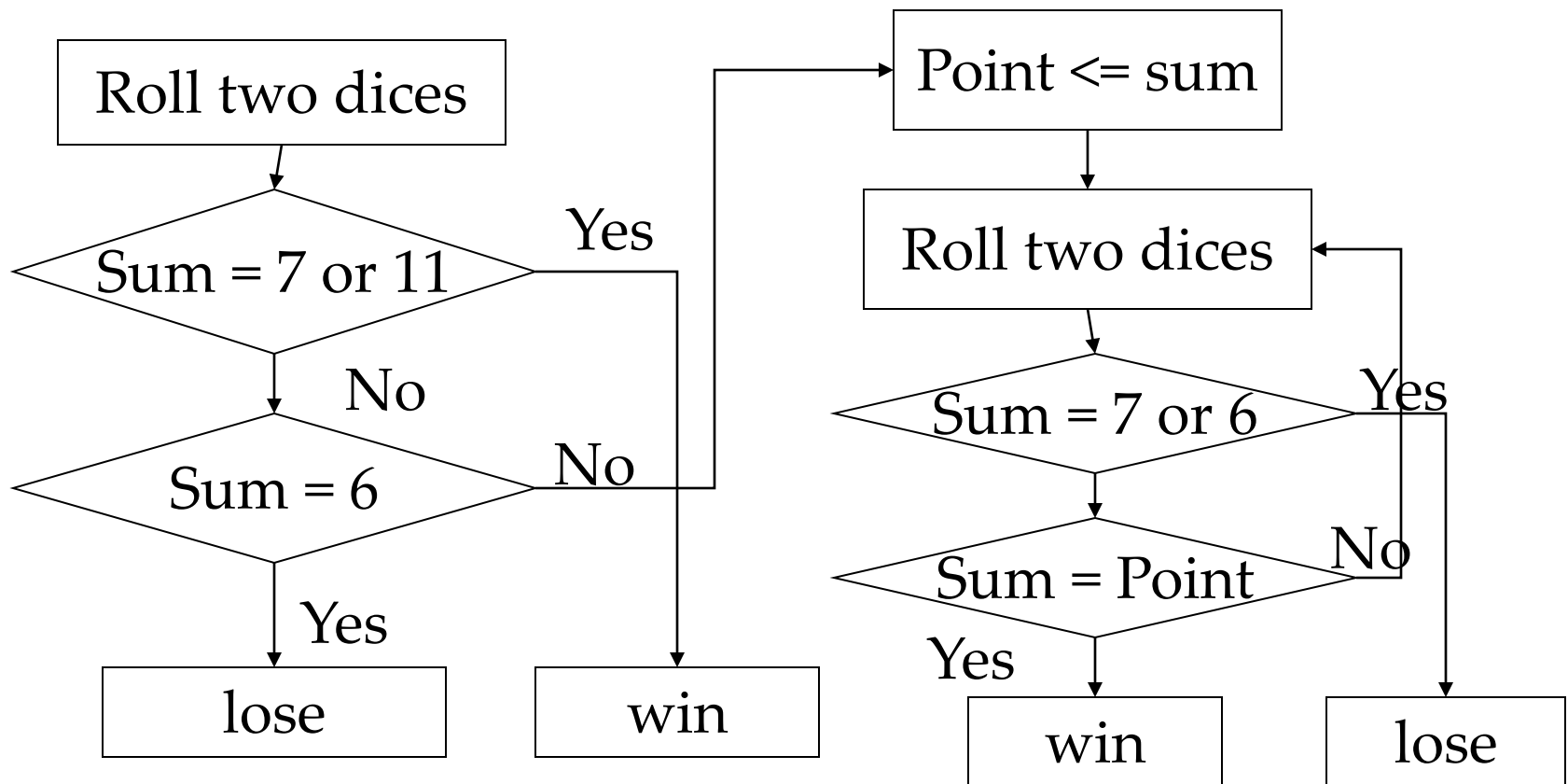



Exercises

1. Design a Dice Game Machine. The game is played with 2 dices. The controller inputs are X, clock, and reset. The outputs are Win, Lose, Dice0[2:0], and Dice1[1:0]. The Flowchart for the game is as follows.




Hints for the Ans (1)

- The Top-Level Submodules

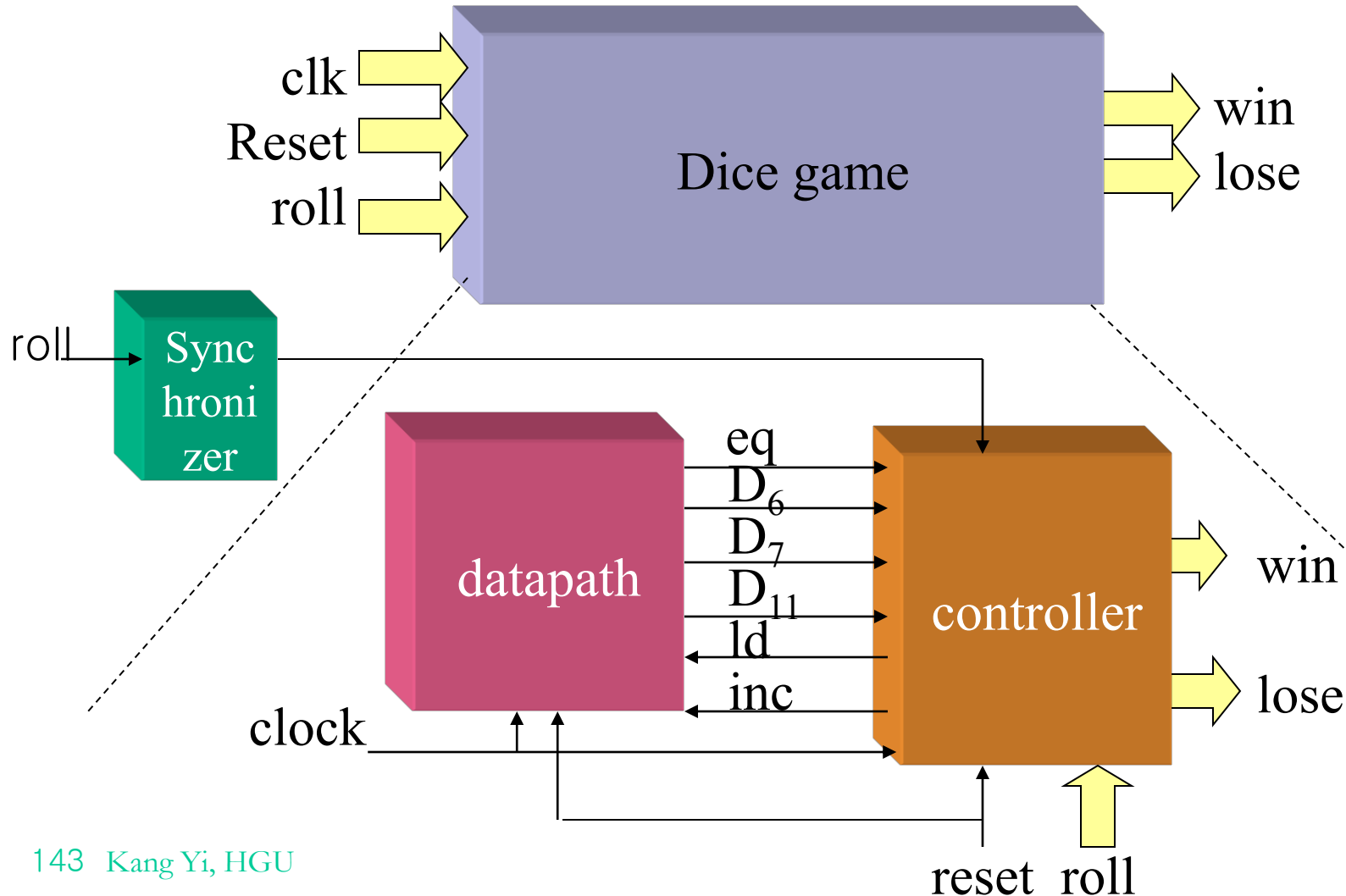


Hints for the Ans (2)

- The Datapath and Control Signals

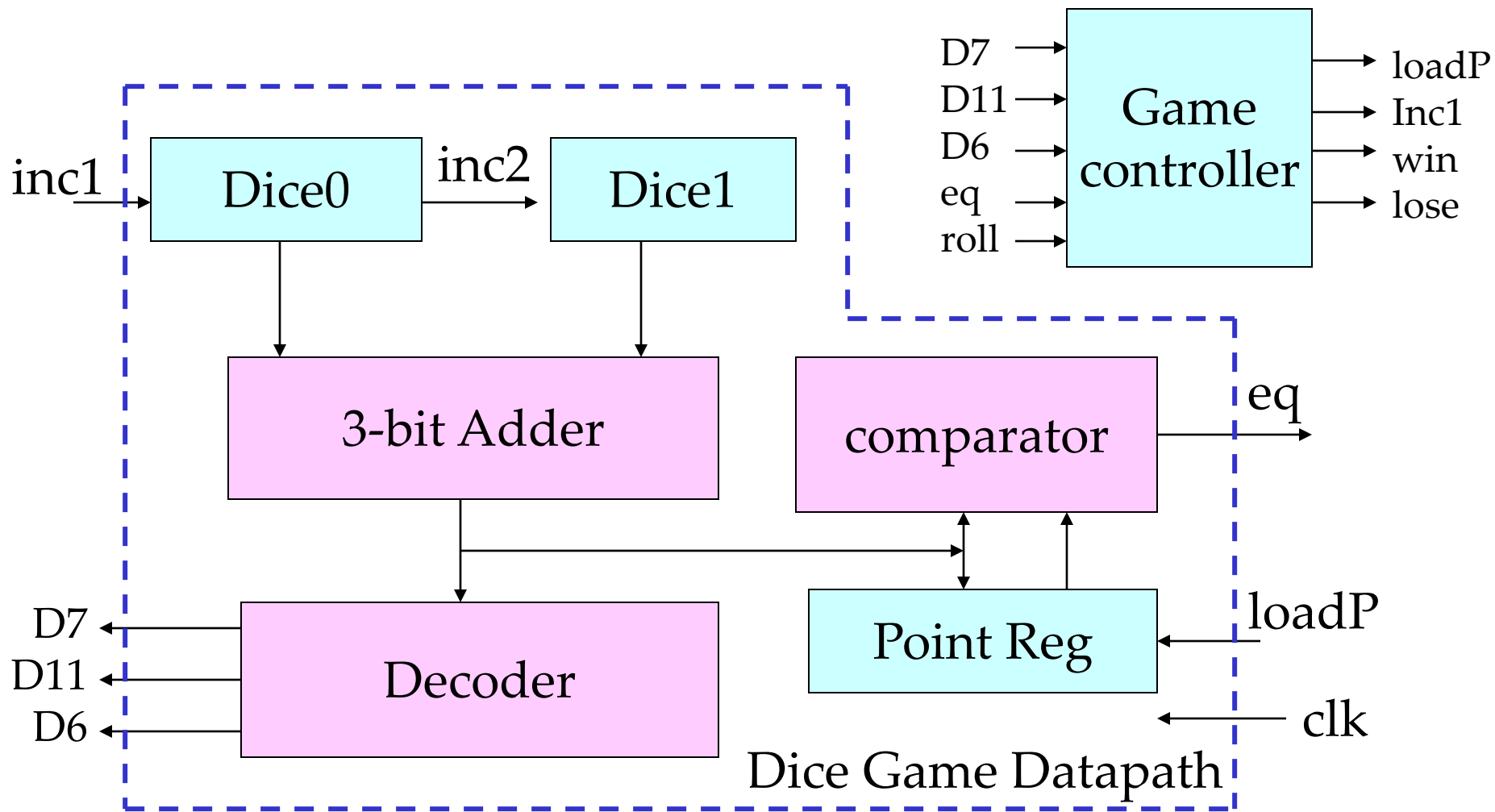

Hints for the Ans (3)

- The Game Controller

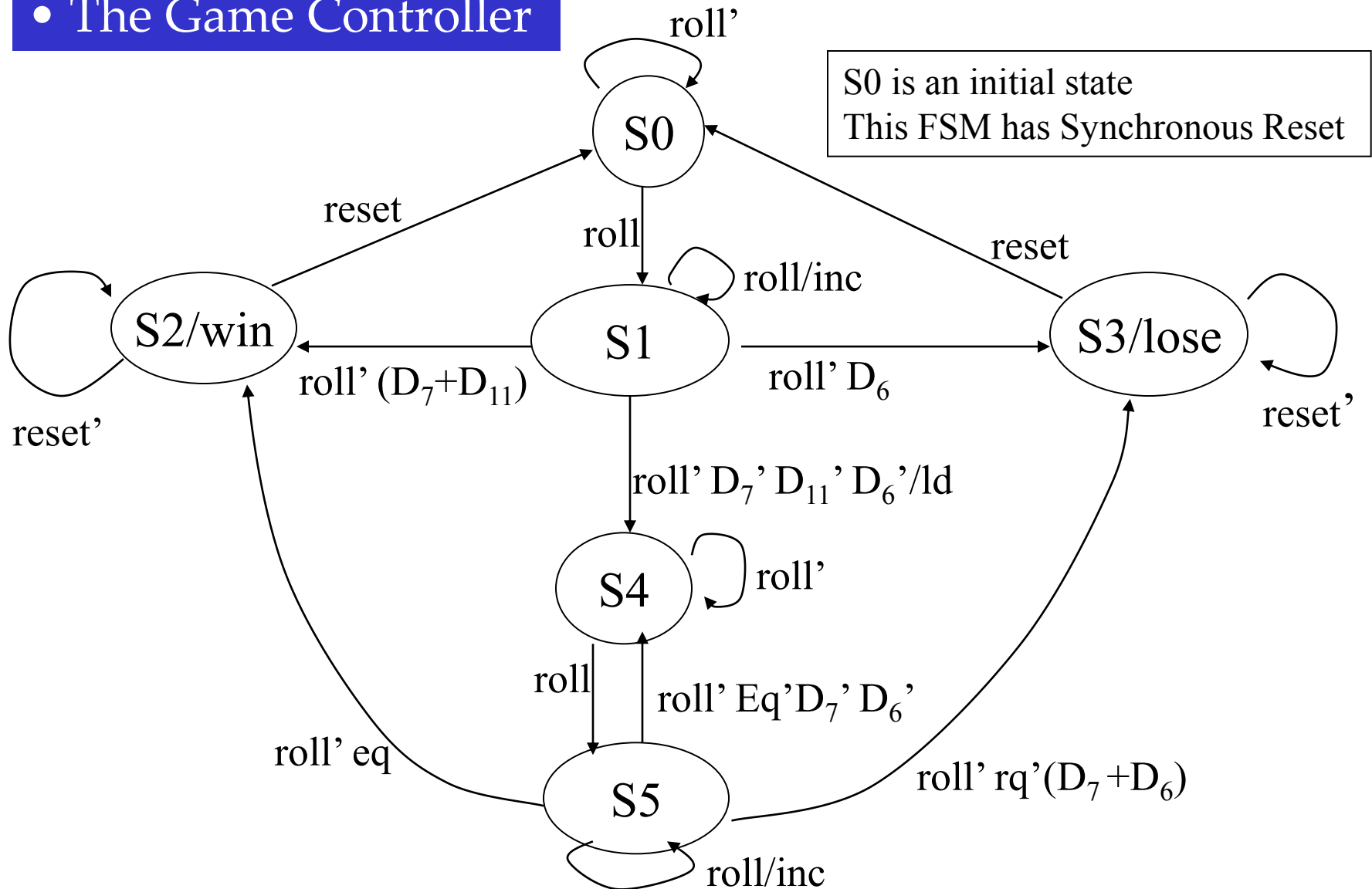

Hints (Synchronizer Design)

- Sometimes Asynchronous Inputs are unavoidable (e.g. User Inputs: roll)
- Asynchronous Inputs : Signals from different Clock Domain
- Synchronizer Objectives : Synchronization & DeBouncing

